

# Homework — 1.4.3 Boolean Algebra

Name: \_\_\_\_\_ Date: \_ **Mark:** \_\_\_\_ / 20

OCR H446 — set after the 1.4.3 lesson. *SHOW ALL WORKING.*

## Part A — This week's topic (~14 marks)

1. Complete the truth table for the expression  $Q = (A + B) \cdot \neg C$ . [3] (AO2)

.....

.....

.....

| A | B | C | A+B | $\neg C$ | Q |
|---|---|---|-----|----------|---|
| 0 | 0 | 0 |     |          |   |
| 0 | 0 | 1 |     |          |   |
| 0 | 1 | 0 |     |          |   |
| 0 | 1 | 1 |     |          |   |
| 1 | 0 | 0 |     |          |   |
| 1 | 0 | 1 |     |          |   |
| 1 | 1 | 0 |     |          |   |
| 1 | 1 | 1 |     |          |   |

2. Use **De Morgan's law** and **double negation** to simplify  $\neg(A \cdot \neg B)$  so that no bar remains over more than one variable. Show each step and name the law used at each step. [2] (AO2)

.....

.....

.....

Working space:

3. Simplify the expression  $A + \neg A \cdot B$  as far as possible, naming the law(s) you use. [2] (AO1/AO2)

.....

.....

.....

Working space:

4. The truth table below shows the output **X** of a logic circuit with inputs **A**, **B** and **C**.

| A | B | C | X |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

(a) Complete the **Karnaugh map** for **X**. **[1]** (AO2)

.....

.....

|       | BC = 00 | BC = 01 | BC = 11 | BC = 10 |
|-------|---------|---------|---------|---------|
| A = 0 |         |         |         |         |
| A = 1 |         |         |         |         |

(b) Draw the groups on your Karnaugh map and use them to write the **simplified Boolean expression** for **X**. **[3]** (AO2)

.....

.....

.....

.....

Working space:

5. State the Boolean expressions for the **Sum** and **Carry** outputs of a **half adder**, and explain why a half adder **cannot** be used on its own to add the middle columns of a multi-bit binary addition. **[2]** (AO1)

.....

.....

.....

Working space:

6. A **D-type flip-flop** is used in a circuit. State what a D-type flip-flop stores, and when its output is able to change. **[1]** (AO1)

---

---

Working space:

---

## Part B — Retrieval: keep it fresh (~6 marks)

---

7. Explain the difference between **symmetric** and **asymmetric** encryption, and state **one** advantage of asymmetric encryption. (1.3) **[3]** (AO1)

---

---

---

---

Working space:

8. Describe how the **round robin** CPU scheduling algorithm works, and state **one** advantage of it. (1.2) **[3]** (AO1)

---

---

---

---

Working space:

---