

Homework — 1.4.3 Boolean Algebra

Name: _____ Date: _____ Mark: _____ / 20

OCR H446 — set after the 1.4.3 lesson. *SHOW ALL WORKING.*

Part A — This week's topic (~14 marks)

1. Match each Boolean law to its identity: write the correct letter in the **Match** column. One letter is not used. [2] (AO1)

Law	Match
Double negation	
De Morgan's law	
Distribution	
Association	
Commutation	

Letter	Identity
A	$\neg(X \cdot Y) = \neg X + \neg Y$
B	$X \cdot (Y + Z) = X \cdot Y + X \cdot Z$
C	$X + Y = Y + X$
D	$(X + Y) + Z = X + (Y + Z)$
E	$\neg(\neg X) = X$
F	$X + \neg X = 1$

2. Complete the truth table for the expression $Q = (A + B) \cdot \neg C$. [3] (AO2)

A	B	C	A+B	$\neg C$	Q
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

3. A student simplifies $Y = \neg(A + \neg B)$. Their working, shown below, contains **two errors**. Identify and correct each error, then write the correct simplified expression for Y. [3] (AO2)

Step 1 (De Morgan's law): $\quad Y = \neg A + \neg(\neg B)$

Step 2 (double negation): $\quad \neg(\neg B) = \neg B$

Step 3 (result): $\quad Y = \neg A + \neg B$

4. Complete the paragraph using words from the word bank. Each word may be used at most once; **three** words are not needed. [3] (AO1)

A half adder adds two single bits. Its Sum output is A _____ B and its Carry output is A _____ B. A half adder cannot add the middle columns of a multi-bit binary addition because it has no _____ input, so a _____ adder — which accepts three inputs — is used for those columns instead. A D-type flip-flop stores _____ and its output is only able to change on a _____.

Word bank: XOR · AND · OR · carry-in · overflow · full · one bit · one byte · clock pulse

5. An alarm circuit has inputs **A**, **B** and **C** and sounds when its output **X = 1**. The truth table below shows X.

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

(a) Complete the **Karnaugh map** for X. [1] (AO2)

	BC = 00	BC = 01	BC = 11	BC = 10
A = 0				
A = 1				

(b) Draw the groups on your Karnaugh map and use them to write the **simplified Boolean expression** for X. [2] (AO2)

Part B — Retrieval: keep it fresh (~6 marks)

6. (1.3.1) Explain the difference between **symmetric** and **asymmetric** encryption, and state **one** advantage of asymmetric encryption. [3] (AO1)

7. (1.2.1) Describe how the **round robin** CPU scheduling algorithm works, and state **one** advantage of it. [3] (AO1)
